 


# Practice Exercises

Topic #03 - d) Introduction to test-benches

# Exercise #1 - Implement a full-adder and test it using a complete test-bench





Inputs			Outputs	
A	B	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

- As a reminder, this is how a full adder looks like
- Use an internal signal at the end of each gate
- Make sure you declare these internal signals

```
ARCHITECTURE architecture_name OF entity_name IS
    [declarations]
BEGIN
    (code)
END architecture_name;
```

## Main program      Test-bench

  

```
entity adder is
  port (
    a,b,cin: in bit;
    s,cout: out bit
  );
end entity adder;

architecture arch of adder is
  signal c,d,e : bit;
begin

  c <= a XOR b;
  s <= c XOR b;
  d <= b AND cin;
  e <= a AND b;
  cout <= d OR e;
end architecture arch;
```

```
entity test_fa is
end;
```

```
architecture bench of test_fa is
  component adder
    port (a, b, cin: in bit;
          s,cout :out bit);
  end component;
```

```
  signal a, b, cin, s, cout: bit;
```

```
begin
```

```
  a  <= '0',
    '1' after 5ns,
    '0' after 10ns,
    '0' after 15 ns;
```


```
  b  <= '0',
    '1' after 5ns,
    '1' after 10ns,
    '0' after 15 ns;
```

```
  cin <= '0',
    '1' after 5ns,
    '1' after 10ns,
    '1' after 15 ns;
```

```
  m: adder port map (a, b, cin, s, cout);
end bench;
```
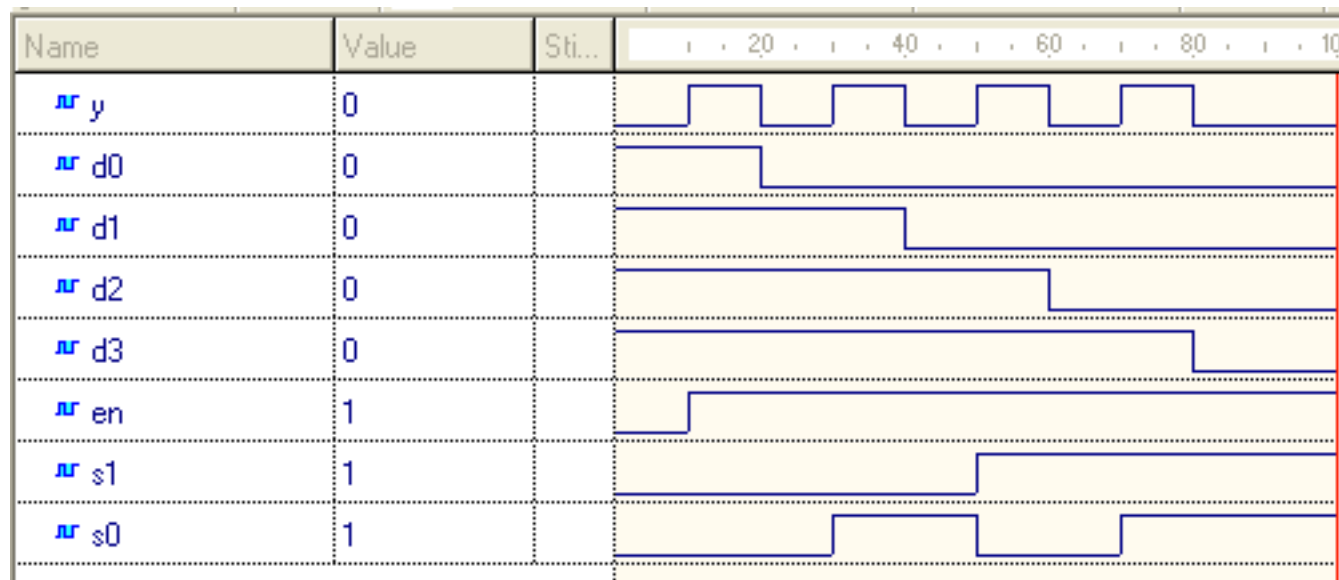
# Exercise #2- Create a test-bench

- What does the code do?
- Create an a test bench that will replicate the following waveforms




```
library IEEE;
use IEEE.std_logic_1164.all;

entity ex3 is
    port (
        en,d3,d2,d1,d0,s1,s0: in STD_LOGIC;
        y: out STD_LOGIC
    );
end entity ex3;

architecture arch of ex3 is
begin
    y<='0' when (en='0') else
        d0 when (s1='0' and s0='0') else
        d1 when (s1='0' and s0='1') else
        d2 when (s1='1' and s0='0') else
        d3;
end architecture arch;
```
 
## The code is for a slightly modified 4-to-1 MUX



```

library IEEE;
use IEEE.std_logic_1164.all;

entity test_ex03 is
end;

architecture testbench of test_ex03 is

component ex03
    port (en, d3, d2, d1, d0, s1, s0: in STD_LOGIC;
          y : out STD_LOGIC);
end component;

signal en, d3, d2, d1, d0, s1, s0, y : STD_LOGIC;

begin
    d0 <= '1', '0' after 20ns;
    d1 <= '1', '0' after 40ns;
    d2 <= '1', '0' after 60ns;
    d3 <= '1', '0' after 80ns;
    en <= '0', '1' after 10ns;
    s1 <= '0', '1' after 50ns;
    s0 <= '0', '1' after 30ns,
        '0' after 60ns,
        '1' after 80ns;

    m: ex03 port map (en, d3, d2, d1, d0, s1, s0, y);

end testbench;

```

# Exercise #3 - Write the main VHDL code from the test-bench + waveform

```
entity testmaincode is
end;
```

```
architecture bench of testmaincode is
  component maincircuit
    port(a,b: in bit;
          z : out bit);
```

```
  end component;
```

```
  signal a,b,z: bit;
```


```
begin
```

```
  a <= '0', '1' after 10ns, '0' after 20ns, '1' after 30ns, '0' after 40ns;
```

```
  b <= '0', '1' after 20ns;
```

```
  m: maincircuit port map (a,b,z);
```

```
end bench;
```

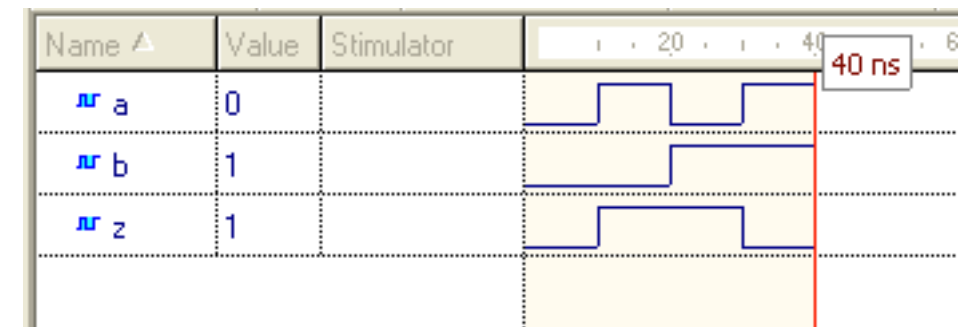

# Solution #3 - Write the main VHDL code from the test-bench + waveform

---

This is just an XOR gate

```
entity maincircuit is
    port(a,b: in bit;
          z : out bit);
end entity;

architecture myarch of maincircuit is
begin
    z <= a XOR b;
end architecture;
```